



One half of the Non-Switching Class-B circuit.

Imagine the compound Q_2 device temperature increased because of a drive signal pulse and the consequent load current.

What does the local feedback loop do to the quiescent current?