

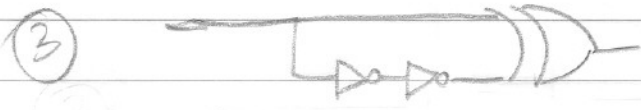
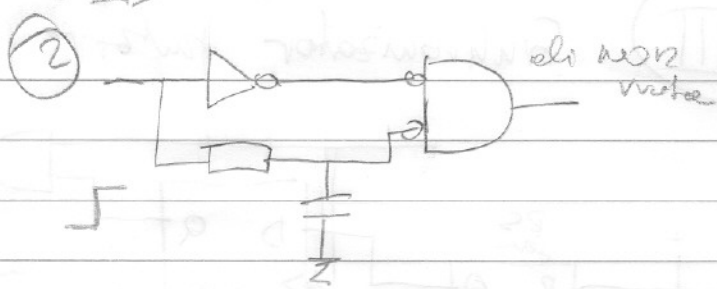


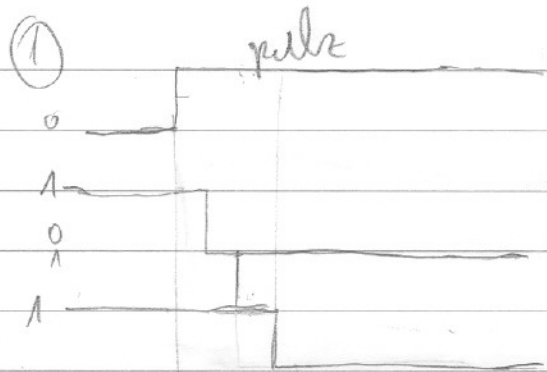→ kaj se zgradí
 a hroto zomejans in minans do
 v = 0




both edge pulse generator

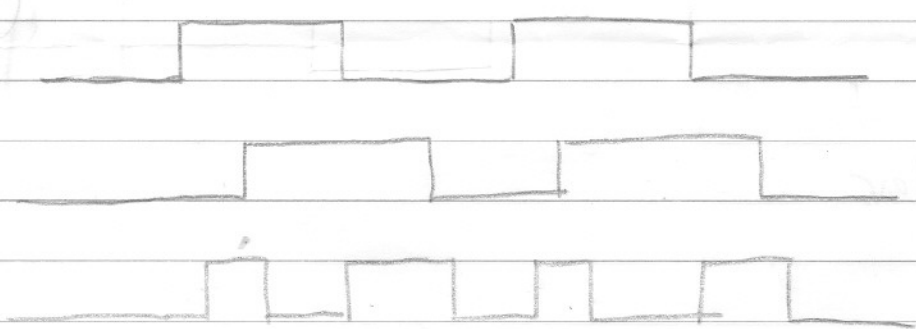

II

S	R	Q_{n+1}
0	0	Q_n
1	0	1
0	1	0
1	1	undefined


J	K	Q_{n+1}
0	0	Q_n
1	0	1
0	1	0
1	1	$\overline{Q_n}$

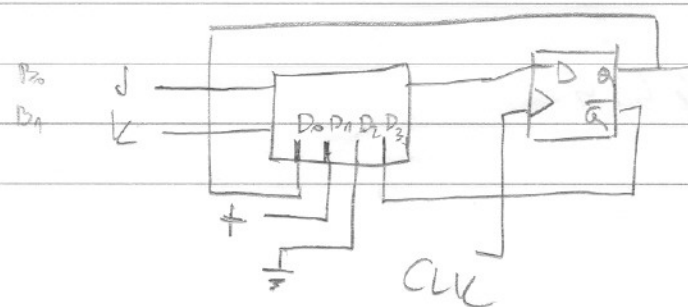


CLK	D	Q_{n+1}
0	0	Q_n
1	0	0
0	1	1



Sinkronizator pulsov

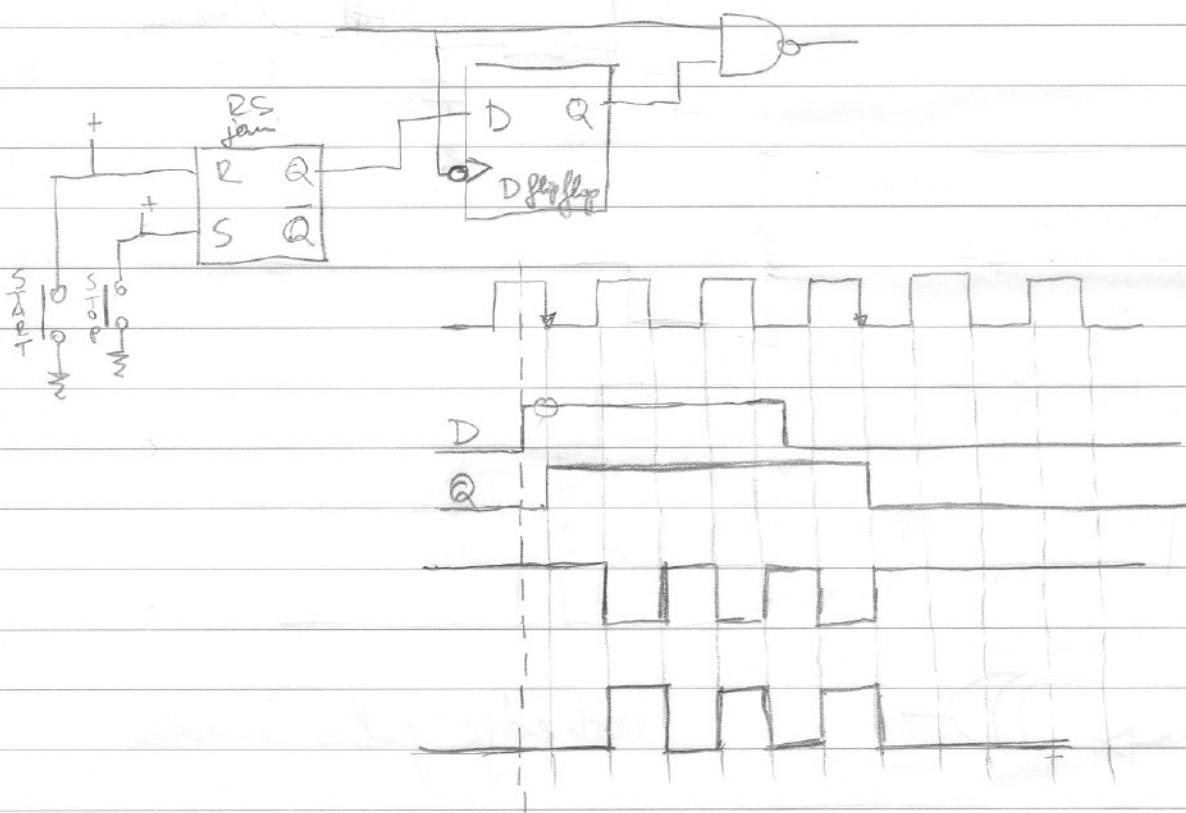


Frequency divider

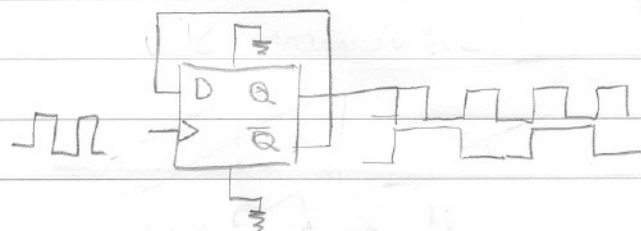

vezore na dve deli dolzi
frekvenco

kako izgleda JK izvedba

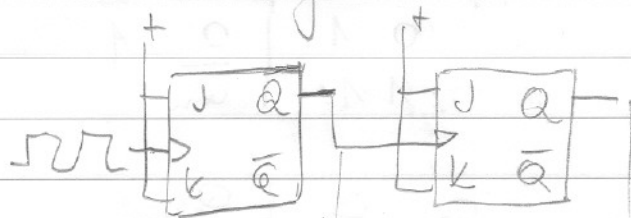

divide by 2

divide by 4