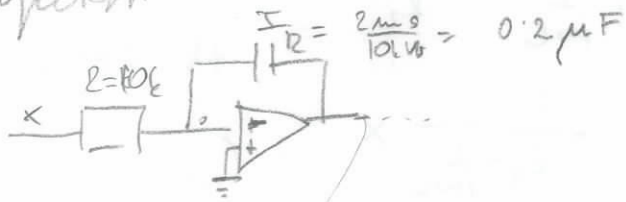


② Sestavke arži s prenosom funkcije $\frac{1}{T_p}$ shodno upravljačtu naj-
 bo 10 kVb avno henderite na 2ms. Ob avn $t=0$
 ste shodna in istodna upravljač 0, nato se shodna
 upravljačt qrenje, kot ji avnons. Nemoj pihel istodna
 upravljačt



$$T = RC$$

$$C = \frac{T}{R}$$


$$\frac{Z}{1} + \frac{x}{Z} = 0$$

$$\frac{1}{pC}$$

$$Z = -\frac{x}{pT}$$


integrator

→ obniti moramo
 si pihel

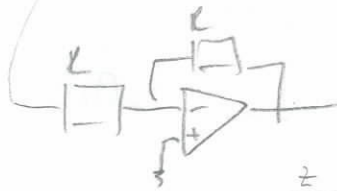

$$\frac{Z}{R} + \frac{x}{C} = 0$$

$$Z = -x$$


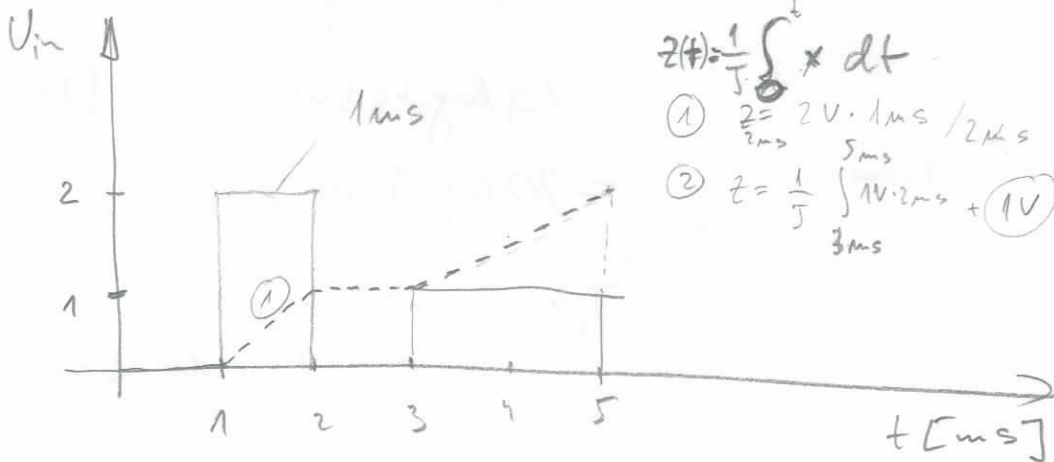


$$Z(t) = \frac{1}{T} \int_0^t x dt$$

① $Z = 2V \cdot 1ms / 2ms$

② $Z = \frac{1}{T} \int_{3ms}^{5ms} 1V \cdot 2ms + 1V \cdot od (1)$

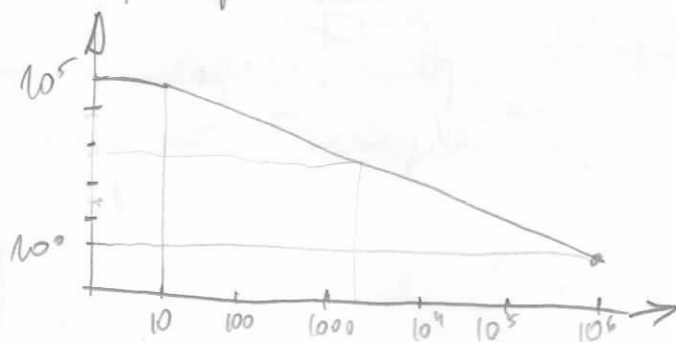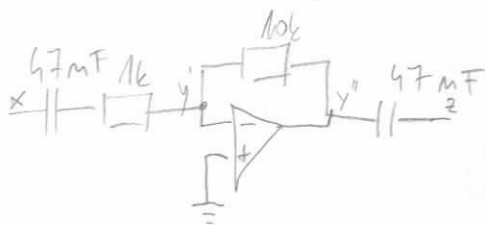- 4) Narysuj funkcję odwrotną opóźnienia w układzie filtra. Na dzień
jaki masz funkcję charakterystyki opóźnienia.



$$\frac{x-y'}{R_1 + \frac{1}{i\omega C}} + \frac{y''-y'}{R_2} = 0$$

$$\frac{y'-y''}{R_2} + \frac{z-y''}{\frac{1}{i\omega C}} = 0 \Rightarrow y' + Ay' + i\omega T_2 (z + Ay') = 0$$

$$A(0-y') = y'$$

$$-Ay' = y''$$

$$y' (1 + A + i\omega T_2 A) = -i\omega T_2 z$$

$$y' = \frac{-i\omega T_2 z}{(1 + A + i\omega T_2 A)}$$

$$x - y' = \left[\frac{R_1}{R_2} + \frac{1}{i\omega T_2} \right] (1 + A) y' = 0$$

$$x = y' \left[1 + \left(\frac{R_1}{R_2} + \frac{1}{i\omega T_2} \right) (1 + A) \right]$$

$$x = \frac{-i\omega T_2 z \left(1 + \left(\frac{R_1}{R_2} + \frac{1}{i\omega T_2} \right) (1 + A) \right)}{(1 + A + i\omega T_2 A)}$$

$$\omega_c / T_2 = 47 \text{mF} \cdot 10 \text{k} \Omega = 2.136 \text{kHz}$$

$$A(\omega_c) \geq 1000$$

pod ω_c

$$\frac{z}{x} = \frac{1 + i\omega T_2}{1 + i\omega T_2 \left(\frac{R_1}{R_2} + 1 \right)}$$

$$20 \log \left| \frac{z}{x} \right| = 20 \log \sqrt{1 + \omega^2 T_2^2} = 20 \log \sqrt{1 + \omega^2 5 \cdot 10^{-5} \frac{R_1^2}{R_2^2}}$$

$$T \cdot \frac{R_1}{R_2} = 10^{-2.5} \Rightarrow \omega_{c1} = 100 \omega_c$$

$$\frac{z}{x} = \frac{1 + A + i\omega T_2 A}{-i\omega T_2 \left[1 + \left(\frac{R_1}{R_2} + \frac{1}{i\omega T_2} \right) (1 + A) \right]}$$


$$\frac{z}{x} = \frac{\frac{1}{A} + 1 + i\omega T_2}{-i\omega T_2 \left[\frac{1}{A} + \left(\frac{R_1}{R_2} + \frac{1}{i\omega T_2} \right) (1 + A) \right]}$$

$$(\omega > 1 \text{MHz}) \quad A \rightarrow 1$$


$$\frac{2 + i\omega T_2}{-i\omega T_2 \left[1 + \left(\frac{R_1}{R_2} + \frac{1}{i\omega T_2} \right) 2 \right]} = \frac{2 + i\omega T_2}{2 + i\omega T_2}$$

$$= 1 + 0.02 i\omega T_2$$

$$20 \log$$

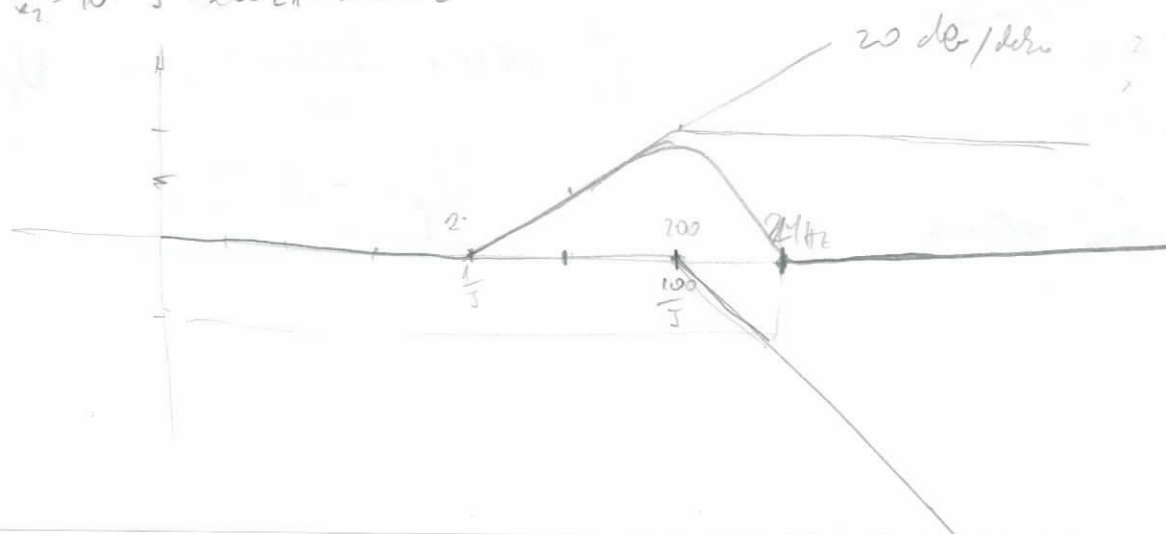

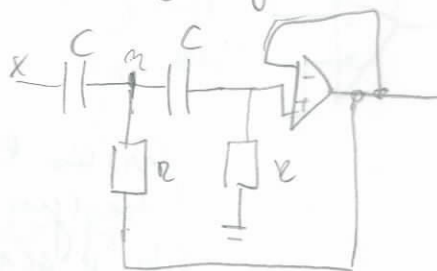2) Zapišite, kako je izračunajete srednje vreme odziva od frekvence vhodnega sinusnega signala.



$$i\omega C(x-z) + \frac{z-z}{R} + (z-z)i\omega C = 0$$

$$i\omega C(z-z) + \frac{0-z}{R} = 0$$

$$i\omega T(z-z) - z = 0$$

$$i\omega Tz - z(1+i\omega T) = 0$$

$$z = \frac{z(1+i\omega T)}{i\omega T}$$

$$i\omega T(x-z) + z-z + i\omega T(z-z) = 0$$

$$-z(2i\omega T + 1) + z(1+i\omega T) + x = 0$$


$$-z \frac{(1+i\omega T)(2i\omega T + 1)}{i\omega T} + z(1+i\omega T) + x = 0$$

$$z(1+i\omega T) \left[1 - \frac{(2i\omega T + 1)}{i\omega T} \right] + x = 0$$

$$z(1+i\omega T) \left[\frac{i\omega T - 2i\omega T - 1}{i\omega T} \right] + x = 0$$

$$z(1+i\omega T) \cdot \frac{-(1+i\omega T)}{i\omega T} + x = 0$$
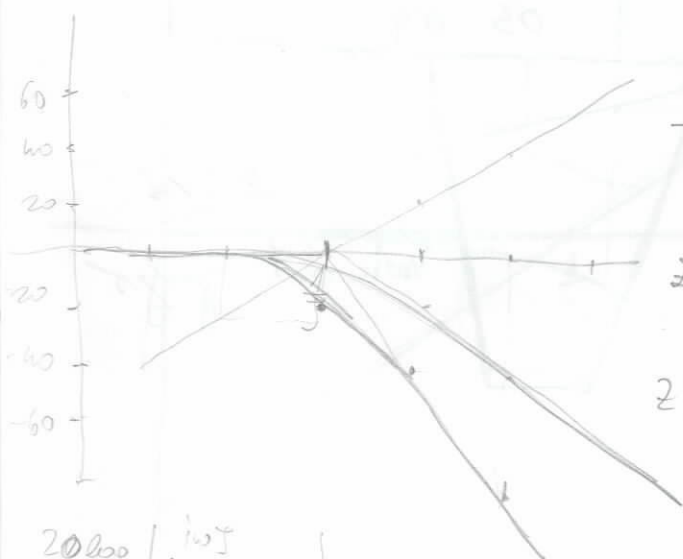
$$\boxed{\frac{z}{x} = \frac{i\omega T}{(1+i\omega T)^2}}$$



$$20 \log \left| \frac{i\omega T}{(1+i\omega T)^2} \right| =$$


$$20 \log \omega T - 40 \log \sqrt{1+(\omega T)^2}$$


$$\arg \varphi = \frac{\ln A}{\ln 4} \Rightarrow \varphi \rightarrow 90^\circ$$

$$\Rightarrow \omega \rightarrow 0; \varphi \rightarrow 0$$

$$\omega = \frac{1}{T}; \varphi = -45 \cdot 2 = -90$$
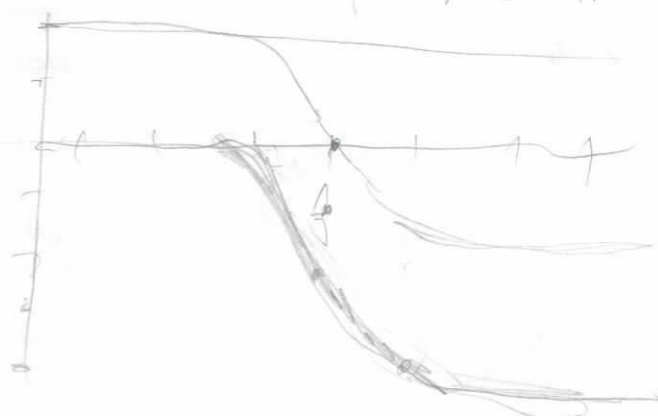
$$\omega \rightarrow \infty; \varphi = -90 \cdot 2 = -180$$



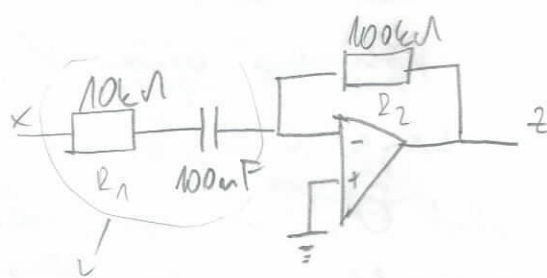


Výhy: Sledí uvoľnenie a odhadmost gainu
je formou samostatného filter

$$Z_s = R_1 + \frac{1}{i\omega C}$$

$$\frac{X}{R_1 + \frac{1}{i\omega C}} + \frac{Z}{R_2} = 0$$

$$Z = -\frac{R_2}{R_1 + \frac{1}{i\omega C}} X$$
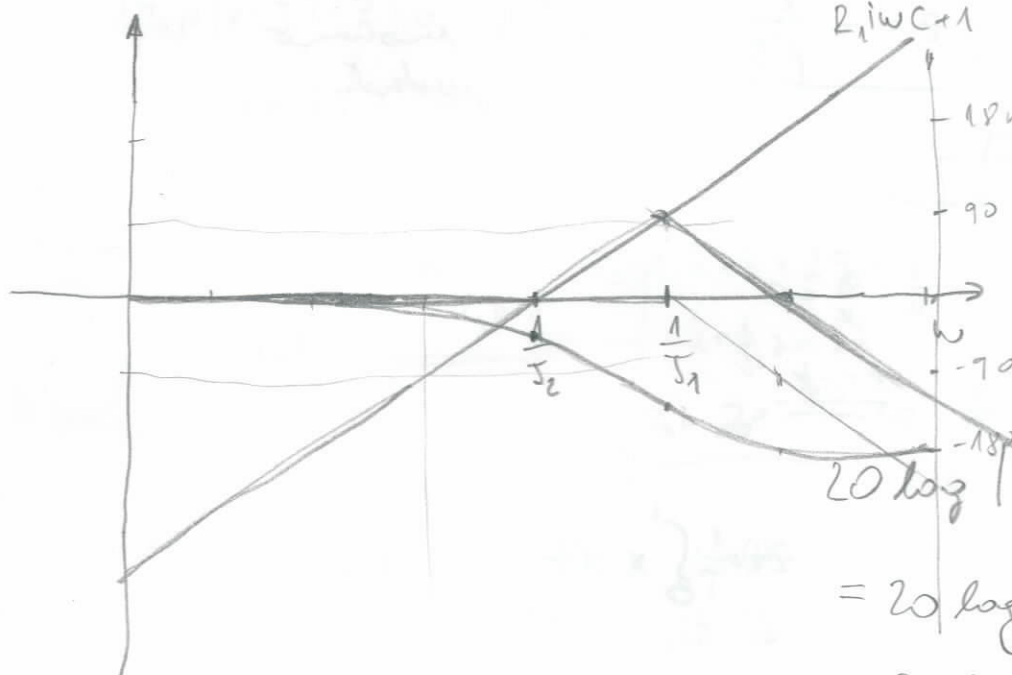
$$Z = -\frac{R_2 i\omega C}{R_1 i\omega C + 1} X = -\frac{R_2 C i\omega}{R_1 i\omega C + 1} X = -\frac{iT_2 \omega}{1 + iT_1 \omega} X$$



$$20 \log \left| \frac{-iT_2 \omega}{1 + iT_1 \omega} \right| =$$

$$= 20 \log |iT_2 \omega| - 20 \log |1 + iT_1 \omega| =$$

$$= 20 \log T_2 \omega - 20 \log \sqrt{1 + T_1^2 \omega^2}$$

Fázor:

$$\tan \varphi = \frac{\text{Im } A}{\text{Re } A}$$

$$\arctan \frac{\text{Im } A}{\text{Re } A} = \varphi$$

① $T_2 \omega$: $\omega \rightarrow 0, \rightarrow \infty$
 $\omega \rightarrow \infty \rightarrow 20 \text{ dB/decade}$

② $T_1 \omega$: $\omega \rightarrow 0, 0$
 $\omega \rightarrow \infty \rightarrow -20 \text{ dB/decade}$

Vlastné fázor:

① $\omega \rightarrow 0 \rightarrow \varphi_1 \rightarrow 0, \varphi_2 \rightarrow 0$

② $\omega \rightarrow \infty \rightarrow \varphi_1 \rightarrow -90^\circ, \varphi_2 = -90^\circ \quad \varphi = \varphi_1 + \varphi_2 = -180^\circ$

③ $\omega = \frac{1}{T_2} \rightarrow \varphi_1 = -45^\circ, \varphi_2 = \arctan -\frac{T_1}{T_2} = -5.6^\circ$
 $\omega = \frac{1}{T_1} \rightarrow \varphi_1 = \arctan -\frac{T_2}{T_1} = -89^\circ, \varphi_2 = -45^\circ$

182/196

③ Starejši op. amp. upravljen v sušidijni vezji, pri čemer lahko $I_B = 0.1 \mu A$ in velik vhod, določeno hitrost pa $S_R = 0.5 V/\mu s$. Na voljo je potek izhodne napetosti $\bar{a}$ pri $C(t=0) = 0$ po tem po. r. $\frac{x}{R} + C_p z = 0$

$$\frac{x}{R} + I_b + C_p z = 0$$

$$x + I_b R + T_p z = 0$$

$$x = -T_p z$$

$$z = -\frac{1}{T_p} \int x dx$$

Določimo hitrost
ne izpreklopa
ker je še vedno
določena hitrost!

$$z = -\frac{1}{T_p} \int (-x - I_b R) dt$$

$$z = -\frac{1}{T_p} \int (x + I_b R) dt$$

$$T = 0.02 s$$

$$I_b R = 0.01 V = 10 mV$$




$$z = -\frac{1}{T_p} [x_0 + I_b R] t$$


$$z = -[x_0 + I_b R] \frac{t}{T_p}$$

$$\left. \begin{aligned} z &= 1.01 V \cdot \frac{0.1 s}{0.02 s} \\ z &= -5.05 V \end{aligned} \right\}$$

$$\left. \begin{aligned} z &= -0.99 V \cdot \frac{0.1 s}{0.02 s} \\ &= 4.95 V \end{aligned} \right\}$$
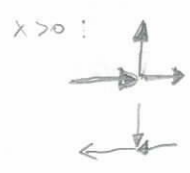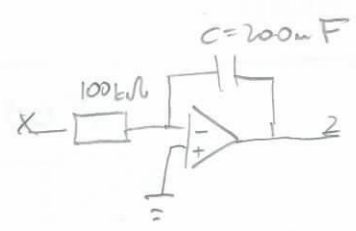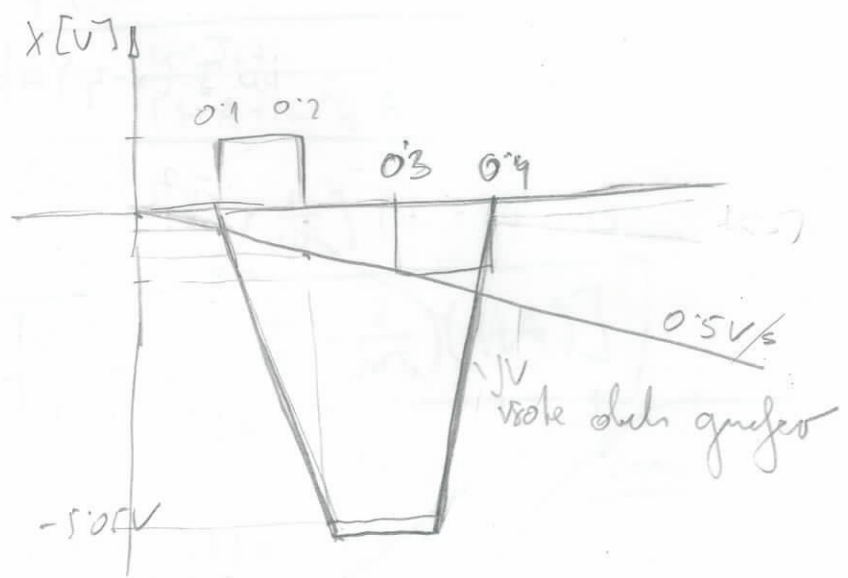
$$\left. \begin{aligned} z &= 0.01 \cdot \frac{0.1 s}{0.02 s} \\ &= 0.05 V \end{aligned} \right\}$$



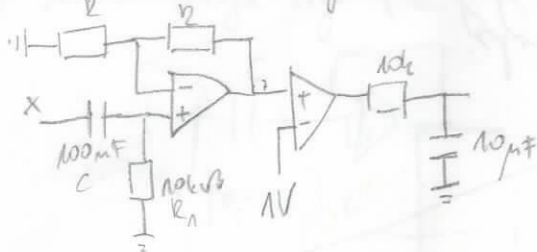

$$\frac{z-y}{R} + \frac{-y}{R} = 0$$

$$z - 2y = 0$$

$$y = \frac{z}{2}$$

$$C_p \left(x - \frac{z}{2} \right) + \frac{-z}{2R_1} = 0$$

$$2T_{1p} \left(x - \frac{z}{2} \right) - \frac{z}{2} = 0$$

$$T_{1p}(2x - z) - z = 0$$

$$-z(T_{1p} + 1) + T_{1p}x = 0$$

prenosna f. ce črna 2

$$\rightarrow z = \frac{2T_{1p}x}{T_{1p} + 1}$$

$$\Rightarrow T_{1p} \dot{z} + z = 2T_{1p} \dot{x}$$

$$T_{1p} = 10k\Omega \cdot 100nF = 1ms$$

$$\dot{z} + \frac{1}{T_{1p}} z = 2\dot{x} \rightarrow$$

$$z_h = z_0 e^{-\frac{1}{T_{1p}} t} \rightarrow z_0 = 2V$$

kot bi videli da je to res 2x
a, ne bi poznali ce črna

$A(z-1)$: $z > 1$ V de dolums +15V

$z < 1$ V de dolums -15V

$$z = z_0 e^{-\frac{t}{T_{1p}}}$$

$$\frac{z_0}{z_0} = e^{-\frac{t}{T_{1p}}}$$

$$\ln \frac{z_0}{z_0} = -\frac{t}{T_{1p}}$$

$$T_{1p} \ln \frac{z_0}{z} = t$$

$$T_{1p} \ln 2 = t$$

absoltna periode: 1ms

$$\frac{t}{t_0}$$

Kaj moramo dungi del vezja:
poravnaji

$$T_p = 10k\Omega \cdot 10\mu F = 0.1s$$

$$\frac{t}{t_0} \cdot 15V + \frac{(t_0 - t)}{t_0} (-15V) = U_p$$

$$U_p = -12.9V$$