

I





	Q_A	Q_B	D_A
$A \rightarrow B$	0	0	1
$B \rightarrow C$	0	1	1
$C \rightarrow A$	1	0	1


00	} A
$Q_A Q_B$	
01	} B
$Q_A Q_B$	
10	} C
$Q_A Q_B$	

$D_A = \overline{Q_A} Q_B = Q_B$ ker imajo shujte "

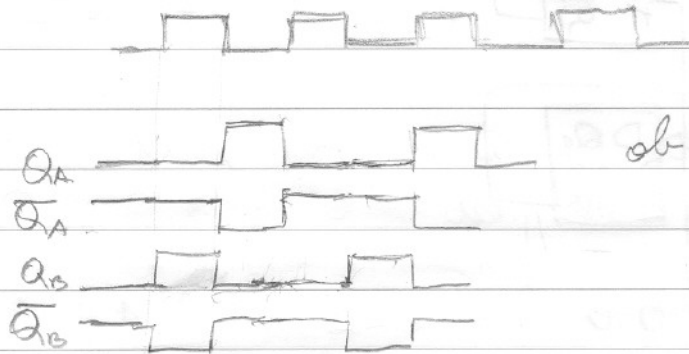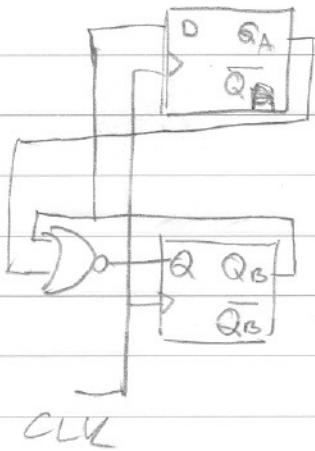
$D_B = \overline{Q_A} \overline{Q_B} = \overline{Q_A + Q_B}$



ob vsaki pulsi


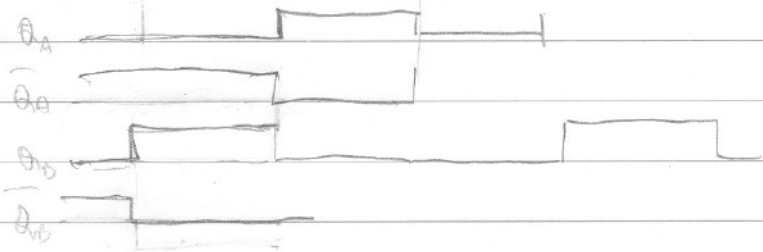


poskusimo naj lažje rešiti

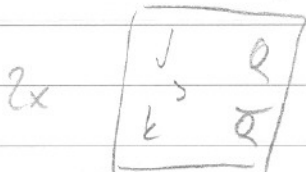

$D_A \rightarrow J_1 K_1$

$D_B \rightarrow J_2 K_2$

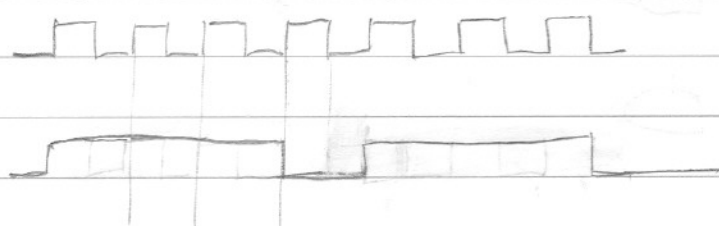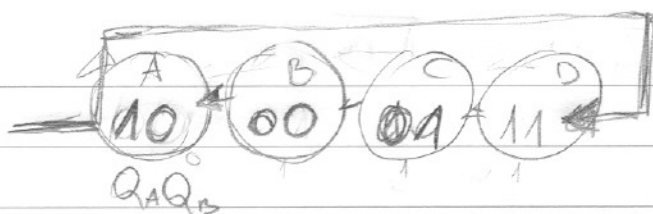

$Q_A = \text{out}$


$B \rightarrow A \rightarrow 0$

	Q_A	Q_B	Q_{out}
$A \rightarrow D$	1	0	1
$D \rightarrow C$	1	1	1
$C \rightarrow B$	0	1	1
$B \rightarrow A$	0	0	0


$$Q_{AD} = \overline{Q_A} \overline{Q_B} + Q_A \overline{Q_B} = \overline{Q_B}$$




$$Q_{BD} = \overline{Q_A} Q_B + Q_A Q_B = Q_A$$

$$Q_{out} = Q_A \oplus Q_B$$

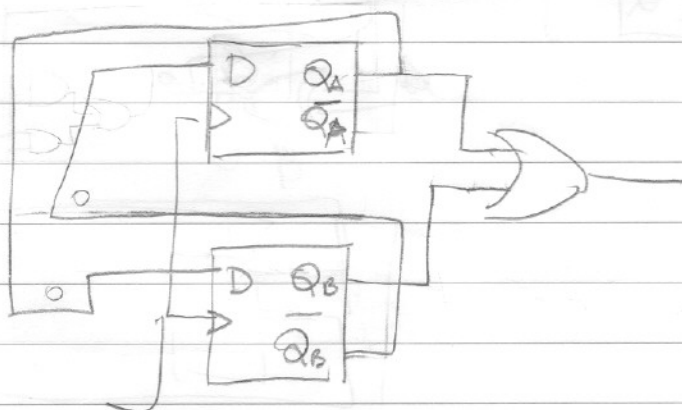

CLK

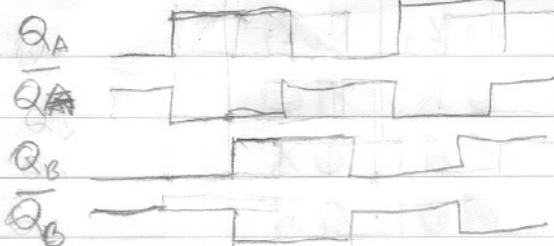


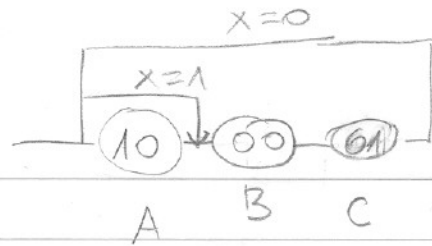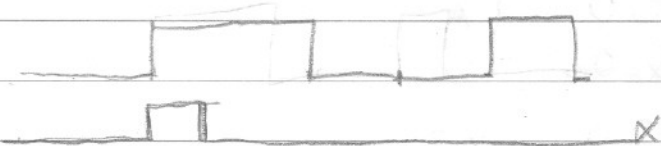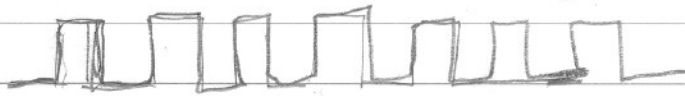

$$D_A = X \cdot Q_A \cdot \bar{Q}_B + \bar{Q}_A \bar{Q}_B$$

$$D_B = \bar{Q}_A \bar{Q}_B$$

	X	Q_A	Q_B
$A \rightarrow A$	1	1	0
$A \rightarrow C$	0	1	0
$C \rightarrow B$	X	0	1
$B \rightarrow A$	X	0	0

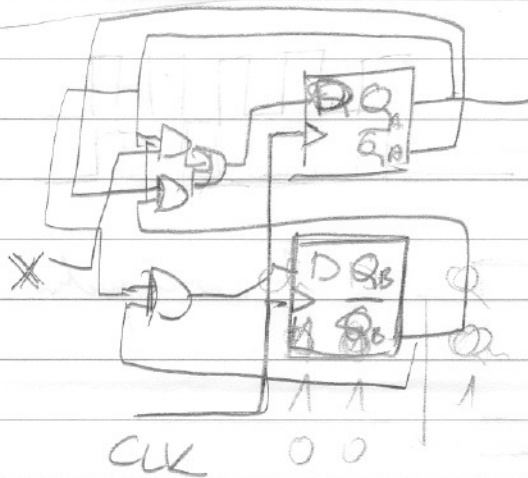

	X	Q_A	Q_B
$A \rightarrow A$	1	1	0
$B \rightarrow A$	X	0	0
$C \rightarrow B$	X	0	1
$A \rightarrow C$	0	1	0

$$Q_A = \bar{Q}_A \bar{Q}_B + X \cdot Q_A \bar{Q}_B$$