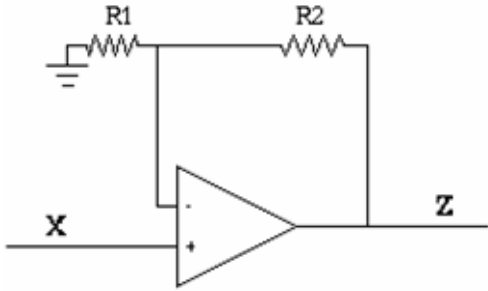


Primer uporabe: ojačevalec , neidealen OP-AMP



$$\frac{0 - \eta}{R_1} + \frac{z - \eta}{R_2} + I_{bias} = 0$$

$$A(x - \eta + Off) = z \Rightarrow \eta = -\frac{z}{A} + Off + x$$

$$\frac{(-x + \frac{z}{A} - Off)}{R_1} + \frac{(z + \frac{z}{A} - Off - x)}{R_2} + I_{bias} = 0$$

$$z \left[\frac{1}{R_2} + \frac{1}{AR_1} + \frac{1}{AR_2} \right] - x \left[\frac{1}{R_1} + \frac{1}{R_2} \right] - Off \left[\frac{1}{R_1} + \frac{1}{R_2} \right] + I_{bias} = 0$$

$$z = \frac{\left[\frac{1}{R_1} + \frac{1}{R_2} \right]}{\left[\frac{1}{AR_1} + \frac{1}{AR_2} + \frac{1}{R_2} \right]} x + Off \frac{\left[\frac{1}{R_1} + \frac{1}{R_2} \right]}{\left[\frac{1}{AR_1} + \frac{1}{AR_2} + \frac{1}{R_2} \right]} - \frac{I_{bias}}{\left[\frac{1}{AR_1} + \frac{1}{AR_2} + \frac{1}{R_2} \right]}$$

$$z = \frac{\frac{R_2}{R_1} + 1}{1 + \frac{1}{A} + \frac{R_2}{AR_1}} x + Off \frac{\frac{R_2}{R_1} + 1}{1 + \frac{1}{A} + \frac{R_2}{AR_1}} - I_{bias} R_2 \frac{1}{1 + \frac{1}{A} + \frac{R_2}{AR_1}}$$

PRIMERI

1.) $A \rightarrow \infty$

$$z = \left[\frac{R_2}{R_1} + 1 \right] x + Off \left[\frac{R_2}{R_1} + 1 \right] - R_2 I_{bias}$$


2.) $Off \rightarrow 0$, $Off \in [\mu V - mV]$

$$z = \left[\frac{R_2}{R_1} + 1 \right] x - R_2 I_{bias}$$

3.) $I_{bias} \rightarrow 0$

$$z = \left[\frac{R_2}{R_1} + 1 \right] x$$

- Seštevalnik (DA konverter)

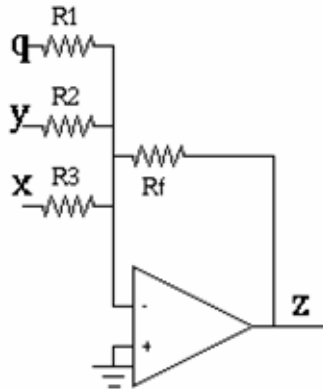

$$A \rightarrow \infty, \text{Off} = 0, I_{bias} = 0$$

$$\frac{q}{R_1} + \frac{y}{R_2} + \frac{x}{R_3} + \frac{z}{R_f} = 0$$

$$z = -R_f \left[\frac{q}{R_1} + \frac{y}{R_2} + \frac{x}{R_3} \right] = - \left[\frac{R_f}{R_1} q + \frac{R_f}{R_2} y + \frac{R_f}{R_3} x \right]$$


PRIMERI

$$1.) R_f = R_1 = R_2 = R_3 \rightarrow z = -(x + y + q)$$

$$2.) \frac{R_f}{R_1} = 1, \frac{R_f}{R_2} = 2, \frac{R_f}{R_3} = 4$$

V 2.) smo dobili 3 bitni DAC pretvornik, ki pa ni najboljša rešitev. To bomo spoznali kasneje.

- Kaj dela to vezje?

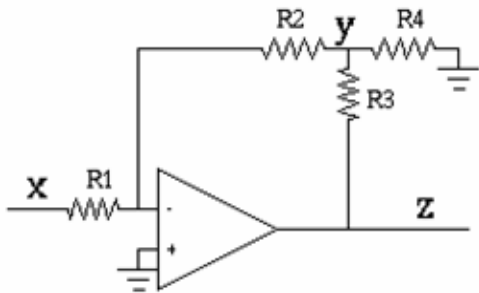

$$\frac{x}{R_1} + \frac{y}{R_2} + I_{bias} = 0$$

$$\frac{z-y}{R_3} + \frac{-y}{R_4} + \frac{-y}{R_2} = 0$$

$$\frac{z + \frac{R_2}{R_1}x + I_{bias}R_2}{R_3} + \frac{\frac{R_2}{R_1}x + I_{bias}R_2}{R_4} + \frac{\frac{R_2}{R_1}x + I_{bias}R_2}{R_2} = 0$$

$$z \frac{1}{R_3} + x \left[\frac{R_2}{R_1 R_3} + \frac{R_2}{R_1 R_4} + \frac{R_2}{R_1 R_2} \right] + I_{bias} \left[1 + \frac{R_2}{R_4} + \frac{R_2}{R_3} \right] = 0$$

$$z = - \left[\frac{R_2}{R_1} + \frac{R_2 R_3}{R_1 R_4} + \frac{R_3}{R_1} \right] x + R_3 I_{bias} \left[1 + \frac{R_2}{R_4} + \frac{R_2}{R_3} \right]$$